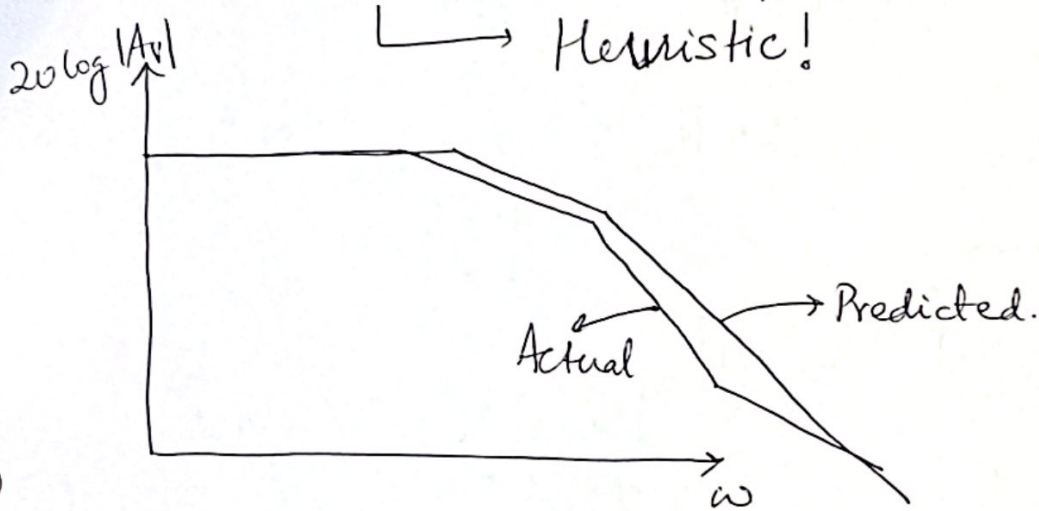


## Lec 22: Frequency Response Analysis


- > Common Source  $\rightarrow$  Two poles & one zero.
- > Poles  $\leftrightarrow$  Nodes method  $\rightarrow$  Two poles



Note:  
Predicted BW  
is higher than  
Actual BW.

- > We want to derive this method of Poles  $\leftrightarrow$  Nodes ~~more~~ rigorously to understand under what conditions is it valid

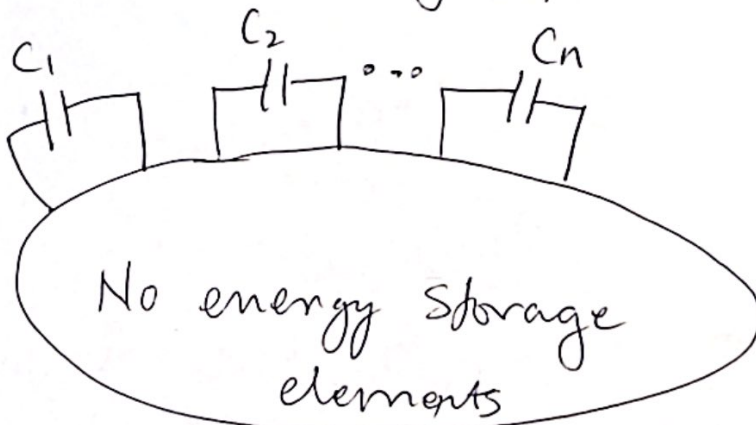- > Assumption 1: Only capacitors in my network.



The transfer function b/w any two circuit quantities

$(V, I)$  is in general:

$$H(s) = A_0 \frac{1 + b_1 s + b_2 s^2 + \dots + b_m s^m}{1 + a_1 s + a_2 s^2 + \dots + a_n s^n} = A_0 \frac{N(s)}{D(s)}$$

$A_0 \rightarrow$  DC gain &  $m < n$ .

$$D(s) = \prod_{k=1}^n \left( 1 - \frac{s}{P_k} \right)$$

If the circuit is stable all poles are in LHP.

Let  $P_k = -\frac{1}{\tau_{P,k}}$  where  $\tau_{P,k} > 0$ .

$$D(s) = \prod_{k=1}^n \left( 1 + s \tau_{P,k} \right) \rightarrow \text{expanding gives}$$


$$= 1 + s \sum_{k=1}^n \tau_{P,k} + s^2 (\dots) + \dots$$

$$\Rightarrow a_1 = \sum_{k=1}^n \tau_{P,k} = - \sum_{k=1}^n \frac{1}{P_k} \left. \begin{array}{l} a_1 \text{ is the sum of} \\ \text{all pole time} \\ \text{constants.} \end{array} \right\}$$

# Open Circuit Time Constant (OCTC) Method

Theorem:  $a_1 = \sum_{i=1}^n \tau_i^0$

↓  
Open Circuit Time Constants.

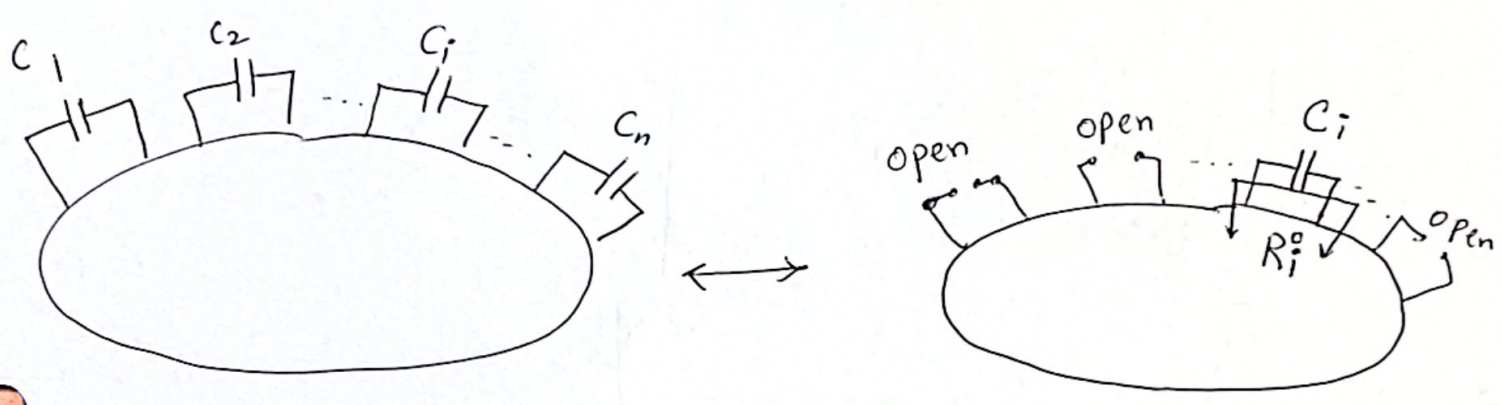

$\tau_i = R_i^0 C_i$

↳ Resistance seen by  $C_i$  when all other caps are open!

NOTE:  $\tau_i^0 \neq \tau_{p,k}$  but the  $\sum$ s are equal.

Proof: From Nodal analysis we can show that

$a_1 = \sum_{i=1}^n \alpha_i C_i$ , then considering one cap at a

time we can show  $\alpha_i = R_i^0$  & use linearity.

(Full proof see Hajimiri's book)

Assumption / Approximation #2 : There is one dominant pole.

$$\Rightarrow |\tau_{p,1}| \gg |\tau_{p,k}|_{k \neq 1}$$

$$\Rightarrow \sum_{k=1}^n \tau_{p,k} \approx \tau_{p,1}$$

$$\Rightarrow \tau_{p,1}^{OCTC} = \sum_{i=1}^n R_i^o C_i$$


$$\Rightarrow \omega_{-3dB}^{OCTC} \approx \frac{1}{\sum_{i=1}^n R_i^o C_i}$$

In exact terms :  $\tau_{p,1}^{exact} = \sum_{i=1}^n R_i^o C_i - \sum_{k=2}^n \tau_{p,k}$

$$\Rightarrow \omega_{-3dB}^{OCTC} \leq \omega_{-3dB}^{actual}$$


This is therefore a conservative estimate of the bandwidth. Earlier poles  $\leftarrow$  nodes overestimated the BW since we also used Miller Approx.

# Common Source (OCTC)

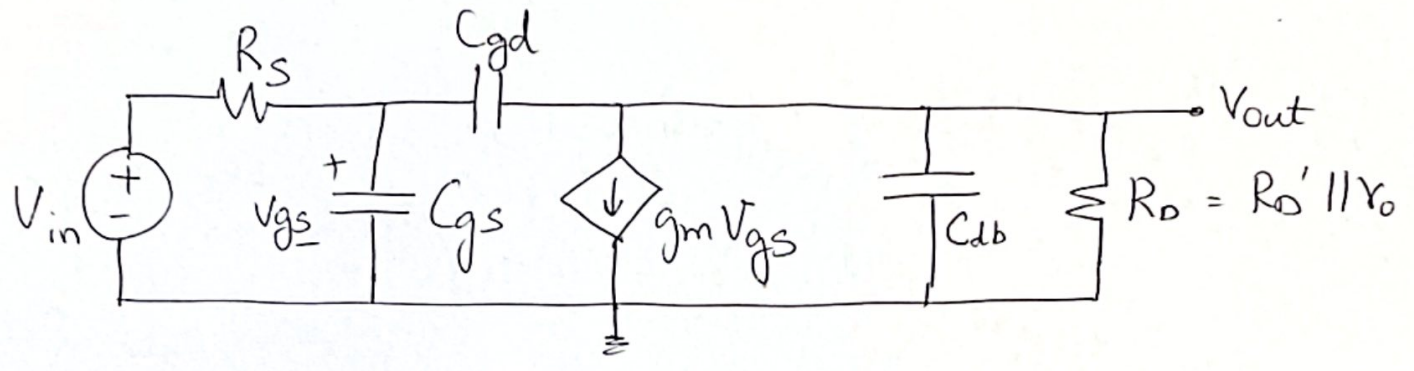

i)  $C_{gs} \therefore R_s$

ii)  $C_{gd} \therefore$

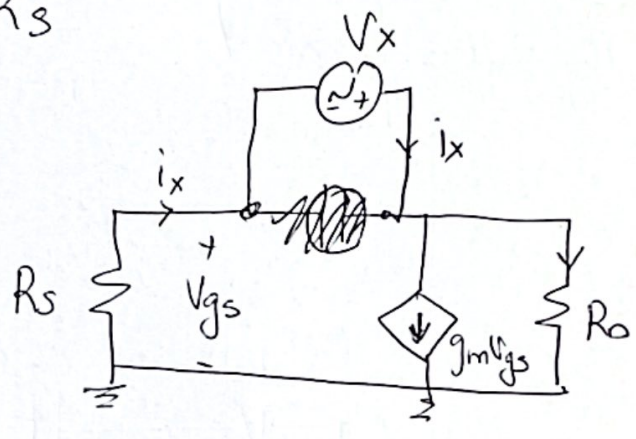

$$\left. \begin{aligned} V_{out} &= (i_x - g_m V_{gs}) R_o \\ V_{gs} &= -i_x R_s \end{aligned} \right\} V_x = (i_x - g_m V_{gs}) R_o + i_x R_s$$

$$\Rightarrow \frac{V_x}{i_x} = (1 + g_m R_s) R_o + R_s$$

iii)  $C_{db} \therefore R_o$

$$\Rightarrow \omega_{PI} = \frac{1}{R_s C_{gs} + (R_s + R_o + g_m R_o R_s) C_{gd} + R_o C_{db}}$$



Recall,  
 Exact sol. with dominant pole approx was

$$\omega \approx \frac{1}{R_s C_{gd} + R_o C_{gd} + (g_m R_o) C_{gd}}$$


$$\omega_{p1} = \frac{1}{R_s (1 + g_m R_o) C_{gd} + R_s C_{gs} + R_o C_{gd} + R_o C_{db}}$$


which is exactly the same!  $\omega_{p1} \approx \frac{1}{R_s (C_{gs} + g_m R_o C_{gd})}$

### Common Drain

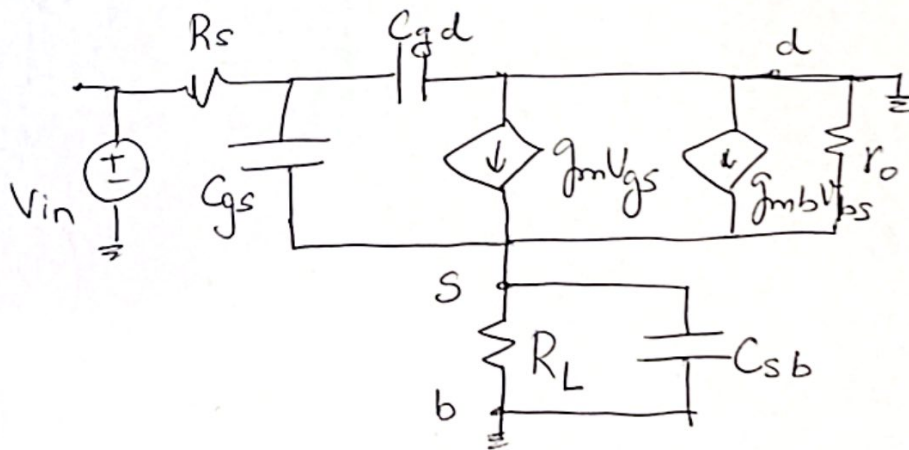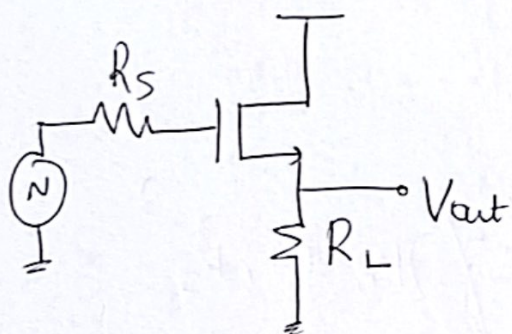

i)  $C_{gs} =$

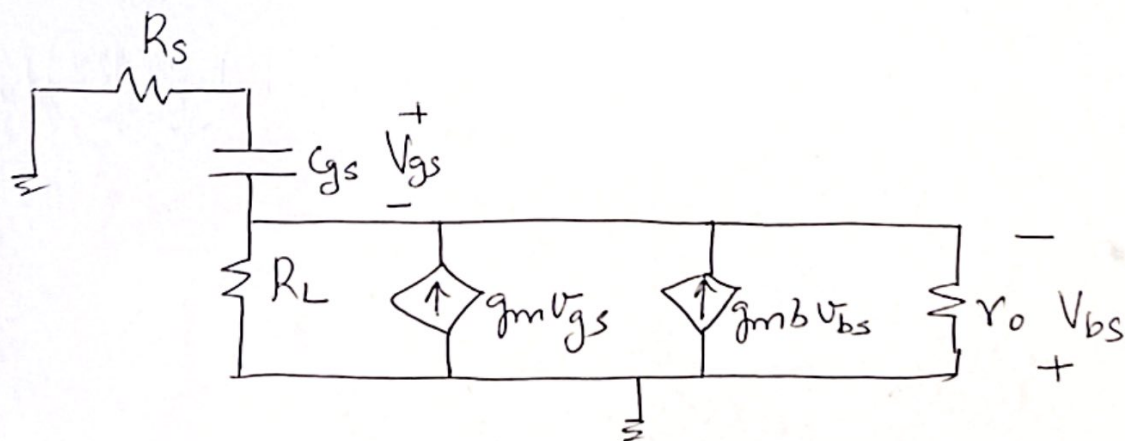

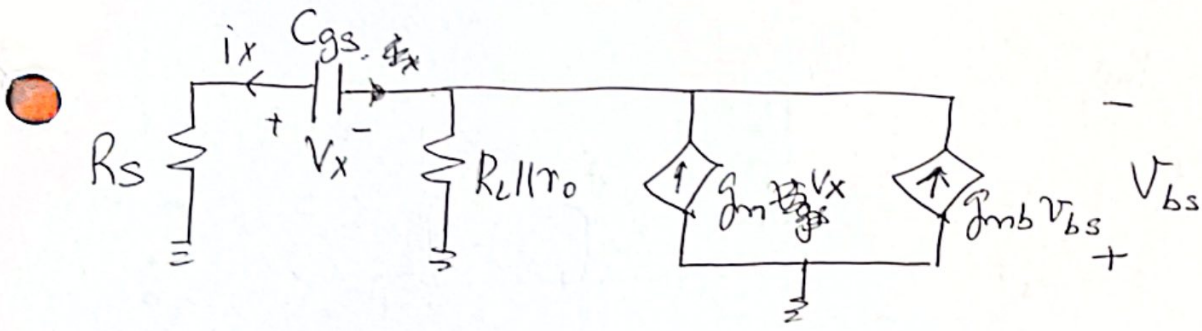

$$-V_{bs} = (-i_x + g_m V_x + g_{mb} V_{bs})(R_L || r_o)$$

$$V_x = (+i_x R_s) + V_{bs} \Rightarrow V_{bs} = V_x - i_x R_s$$


$$\Rightarrow -V_x + i_x R_s = [-i_x + g_m V_x + g_{mb}(V_x - i_x R_s)](R_L || r_o)$$

$$\Rightarrow V_x (g_m (R_L || r_o) + g_{mb} (R_L || r_o) + 1)$$



$$= i_x (+ R_L || r_o + R_s)$$

$$\Rightarrow R_x = \frac{R_s + R_L || r_o}{1 + (g_m + g_{mb})(R_L || r_o)} = R_{gs}^o$$


ii)  $C_{gd}$ :

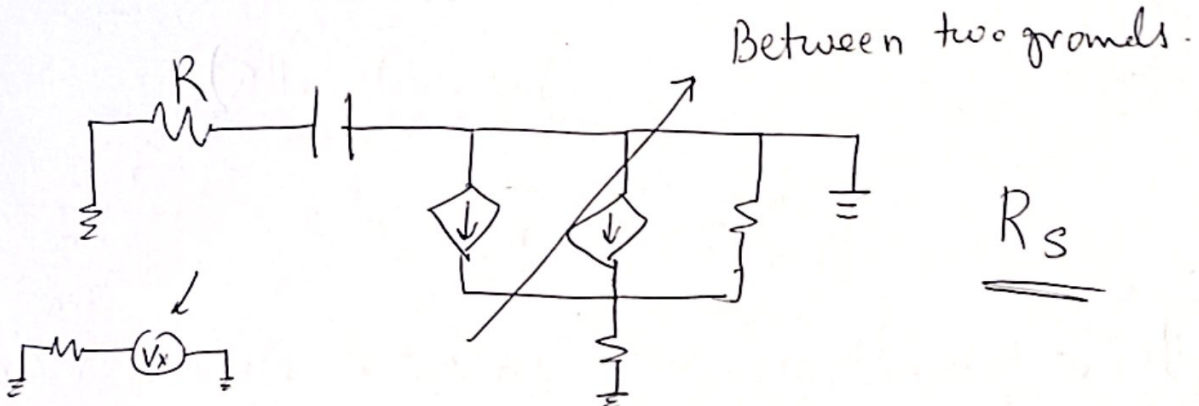

$C_{sb} \Rightarrow$

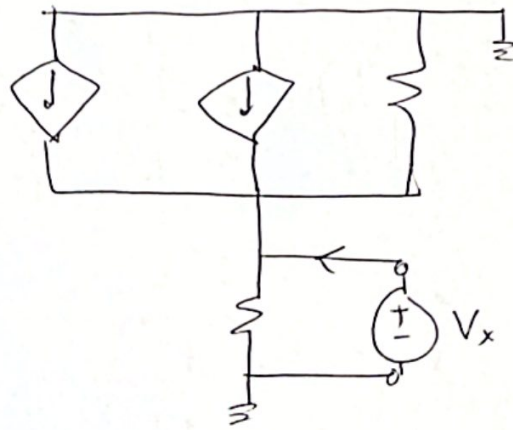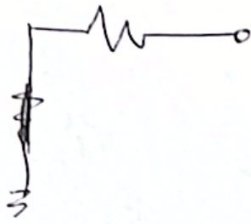

$\Rightarrow$

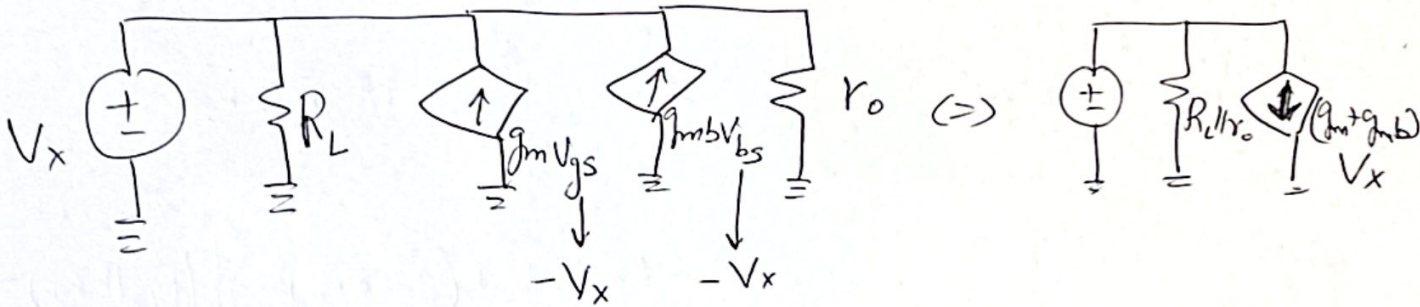

$$\Rightarrow R_{sb}^0 = R_L \parallel r_o \parallel \frac{1}{g_m + g_{mb}}$$

$$\Rightarrow \omega_{3dB} = \frac{1}{R_s C_{gd} + R_{gs}^0 C_{gs} + R_{sb}^0 C_{sb}}$$



Where  $R_{gs}^0 = \frac{R_s + R_L \parallel r_o}{1 + (g_m + g_{mb})(R_L \parallel r_o)} \approx \frac{R_L + R_s}{g_m R_L}$

$R_{sb}^0 \approx R_L \parallel r_m$   $\omega_{3dB} \approx \frac{1}{R_s C_{gd} + \frac{C_{gs}}{g_m}}$   $\approx \frac{1}{g_m}$

No Miller multiplication & all time const. are small  $\Rightarrow$  Large BW!